


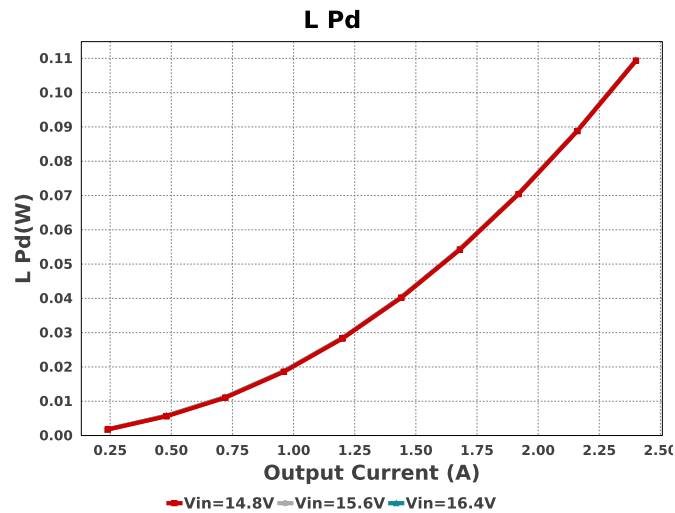
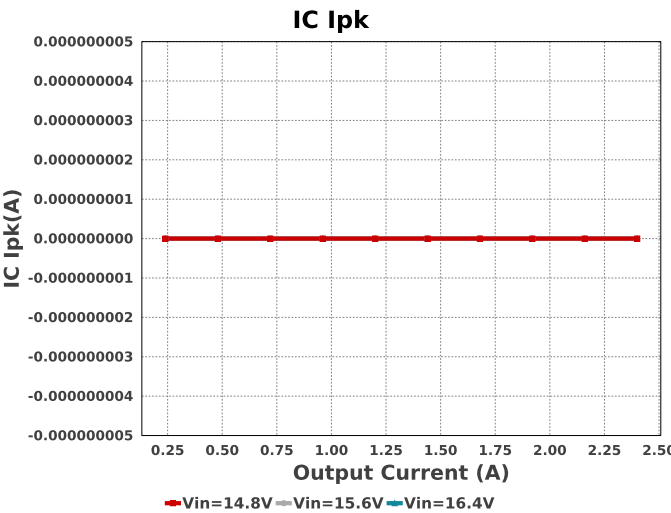
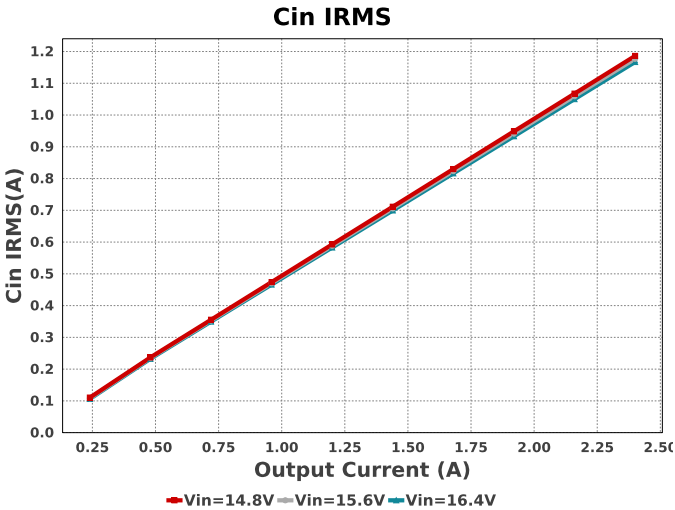
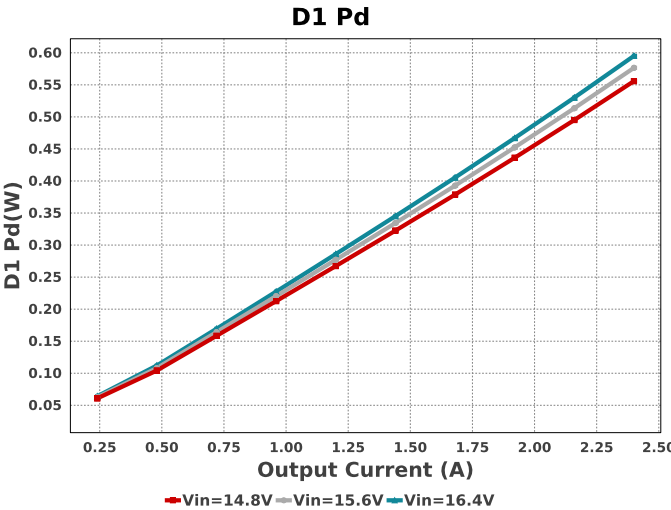
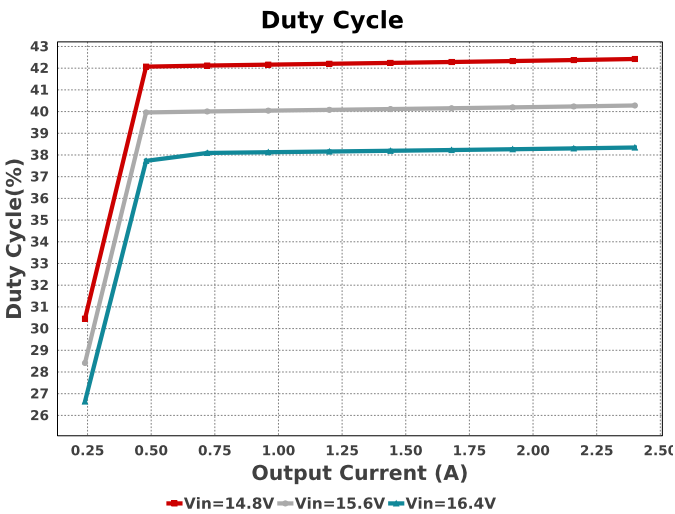
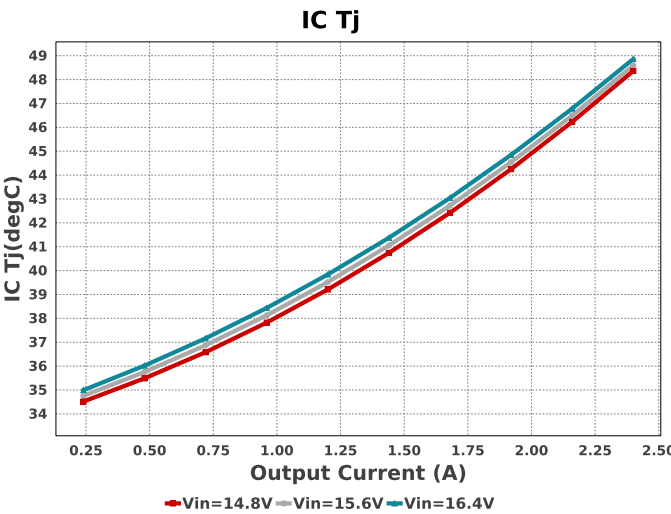
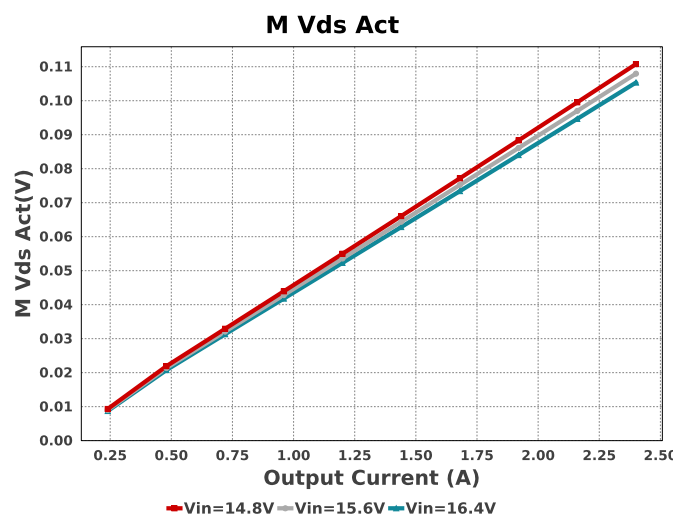
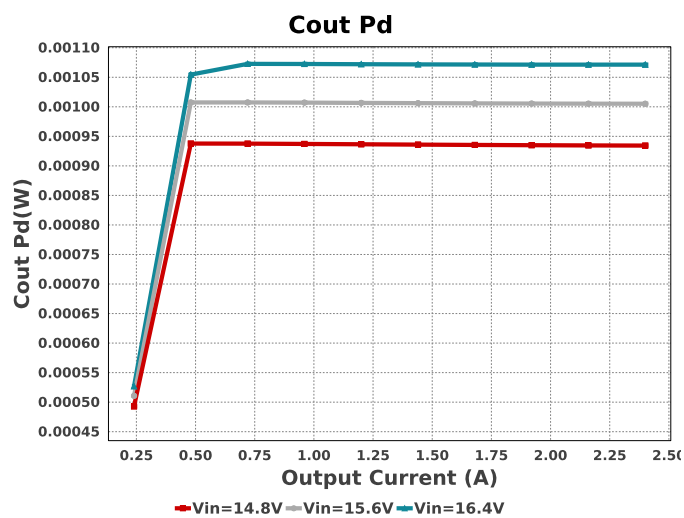
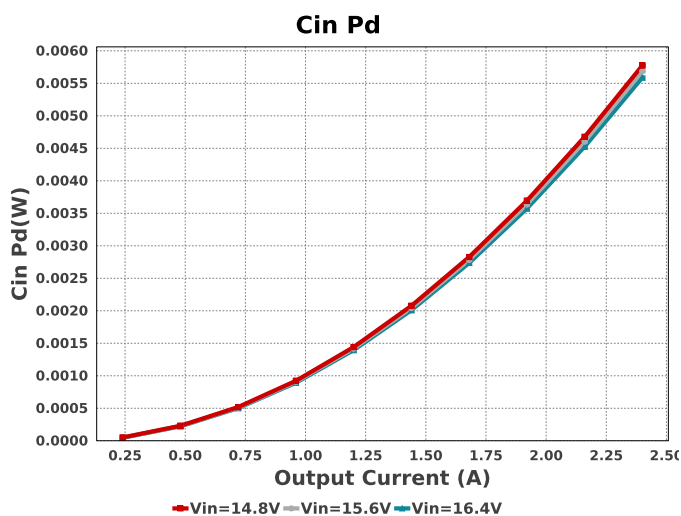







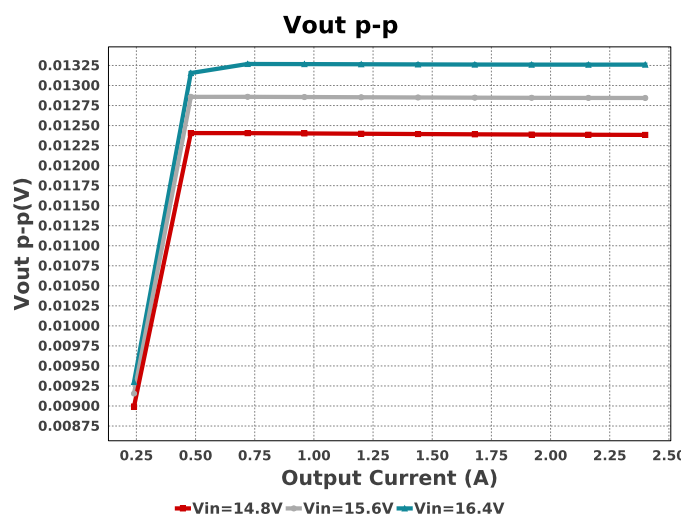



Device = LMR14030SDDAR
Topology = Buck
Created = 2025-08-09 07:12:57.782
BOM Cost = \$3.13
BOM Count = 13
Total Pd = 1.16W

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
U1	Texas Instruments	LMR14030SDDAR	Switcher	1	\$1.21	 DDA0008E_N 55 mm²

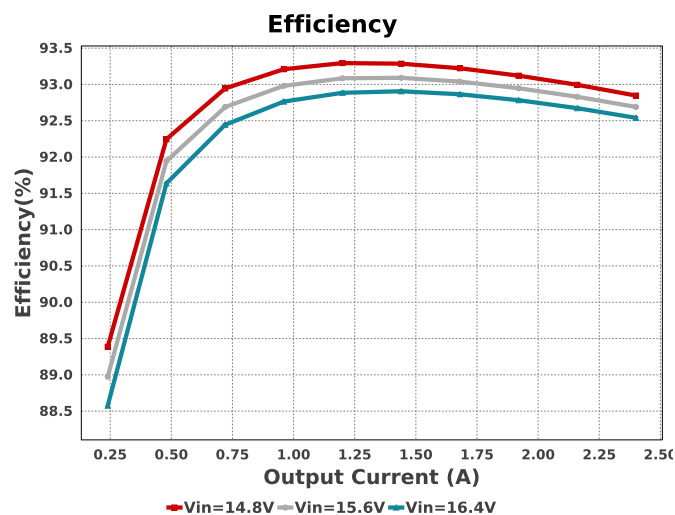

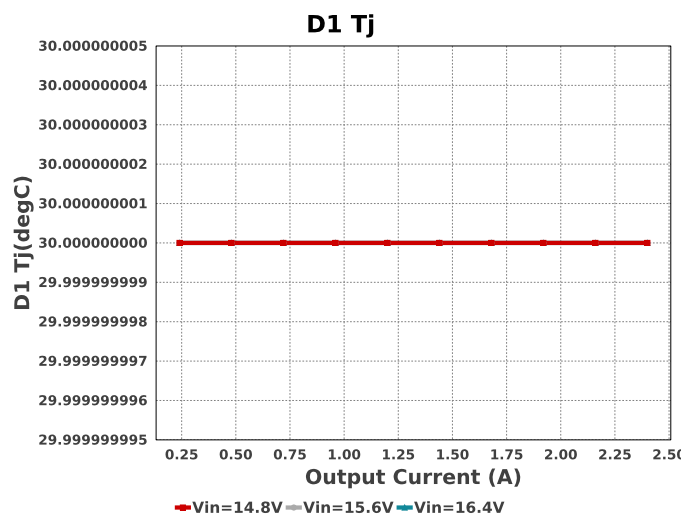

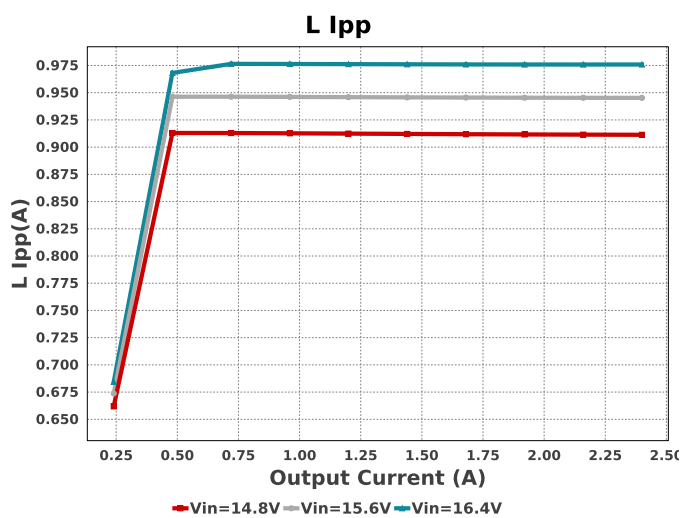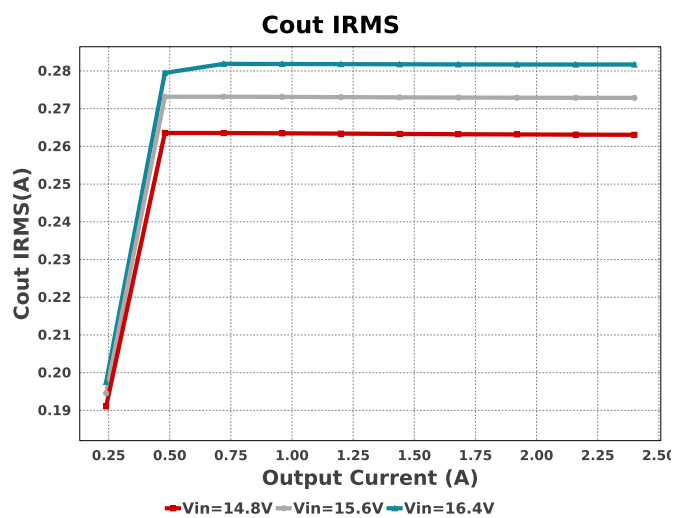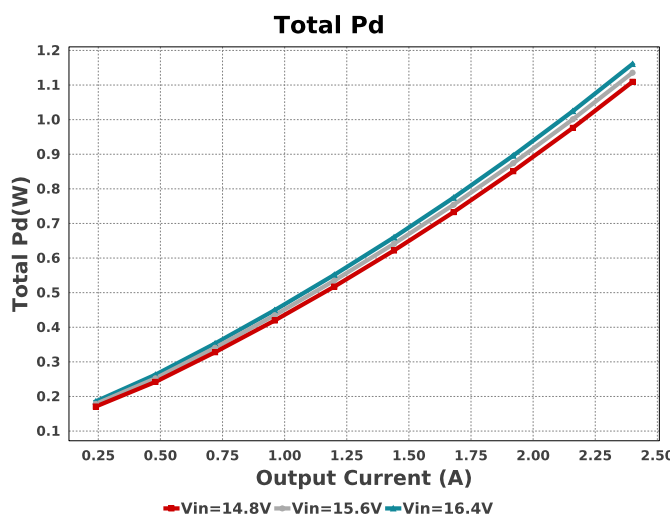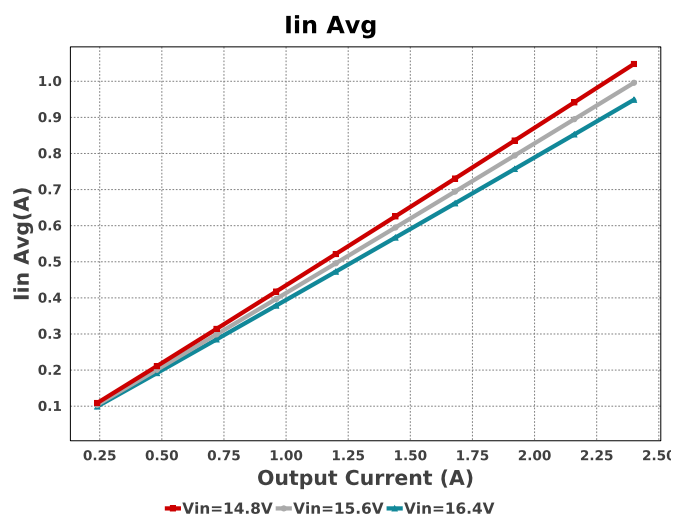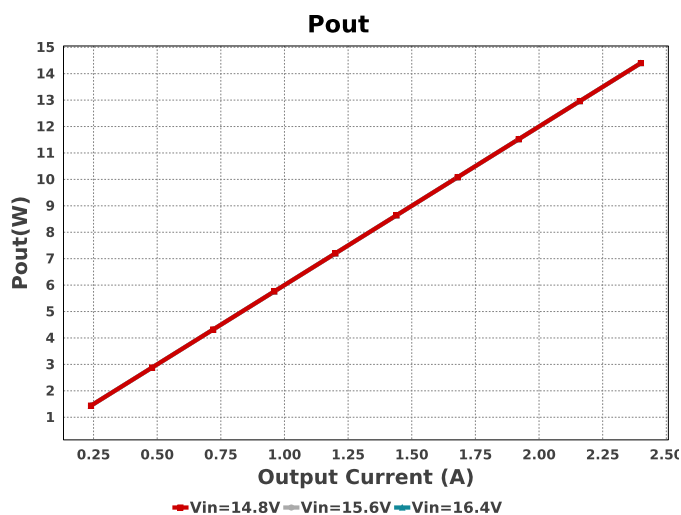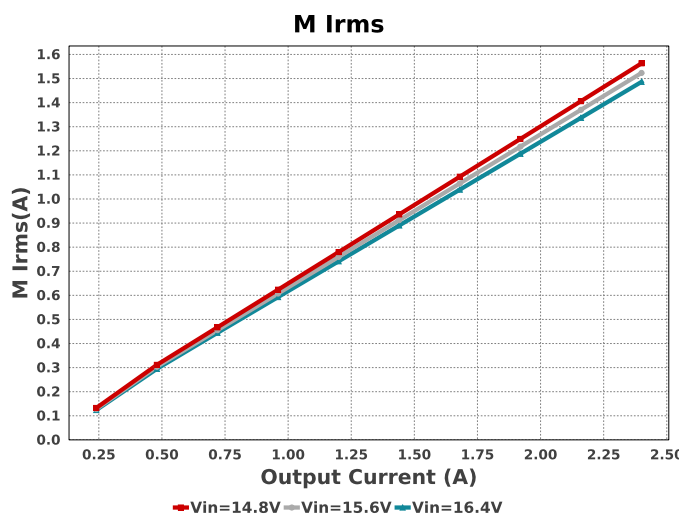

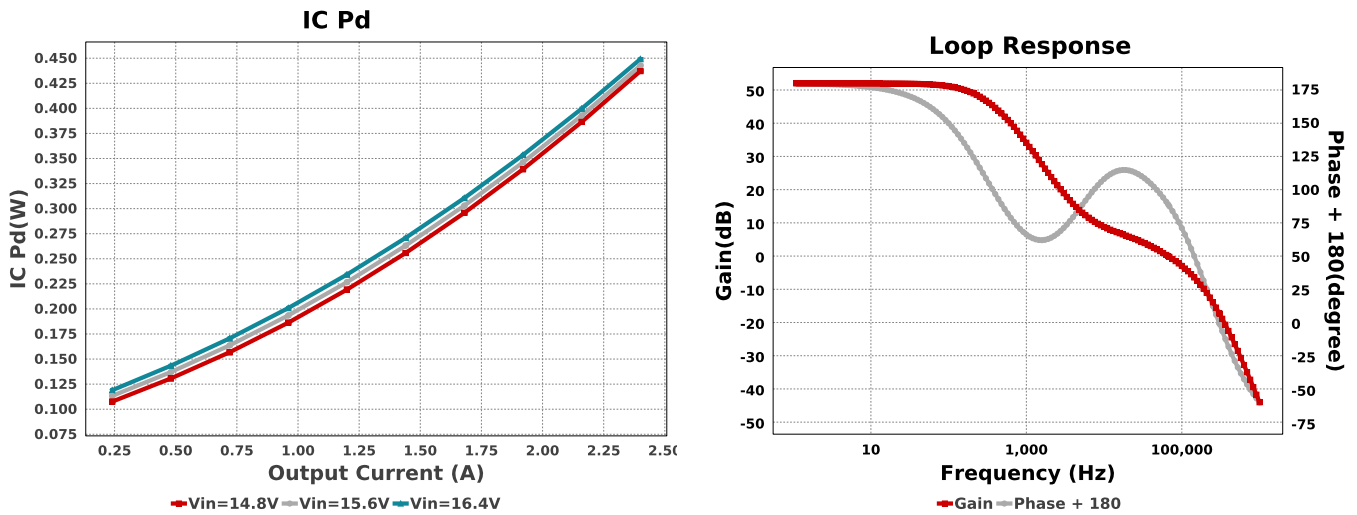

Operating Values

#	Name	Value	Category	Description
1.	BOM Count	13		Total Design BOM count
2.	Total BOM	\$3.13		Total BOM Cost
3.	Cin IRMS	1.167 A	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	5.589 mW	Capacitor	Input capacitor power dissipation
5.	Cout IRMS	281.719 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	1.071 mW	Capacitor	Output capacitor power dissipation
7.	D1 Pd	595.22 mW	Diode	Output Diode Power Dissipation
8.	D1 Tj	30.0 degC	Diode	D1 junction temperature
9.	IC Ipk	0.0 A	IC	Peak switch current in IC
10.	IC Pd	449.11 mW	IC	IC power dissipation
11.	IC Tj	48.862 degC	IC	IC junction temperature
12.	IC Tolerance	18.0 mV	IC	IC Feedback Tolerance
13.	ICThetaJA	42.0 degC/W	IC	IC junction-to-ambient thermal resistance
14.	Iin Avg	948.83 mA	IC	Average input current
15.	L Ipp	975.903 mA	Inductor	Peak-to-peak inductor ripple current
16.	L Pd	109.49 mW	Inductor	Inductor power dissipation
17.	M Irms	1.486 A	Mosfet	MOSFET RMS ripple current
18.	M Vds Act	105.342 mV	Mosfet	Voltage drop across the MosFET
19.	Cin Pd	5.589 mW	Power	Input capacitor power dissipation
20.	Cout Pd	1.071 mW	Power	Output capacitor power dissipation
21.	D1 Pd	595.22 mW	Power	Output Diode Power Dissipation
22.	IC Pd	449.11 mW	Power	IC power dissipation
23.	L Pd	109.49 mW	Power	Inductor power dissipation
24.	Total Pd	1.161 W	Power	Total Power Dissipation
25.	Cross Freq	66.653 kHz	System	Bode plot crossover frequency
26.	Duty Cycle	38.344 %	System	Duty cycle
27.	Efficiency	92.54 %	System	Steady state efficiency
28.	FootPrint	391.0 mm ²	System	Total Foot Print Area of BOM components
29.	Frequency	493.274 kHz	System	Switching frequency
30.	Gain Marg	-17.365 dB	System	Bode Plot Gain Margin
31.	Iout	2.4 A	System	Iout operating point
32.	Low Freq Gain	51.975 dB	System	Gain at 1Hz
33.	Mode	CCM	System	Conduction Mode
34.	Phase Marg	89.367 deg	System	Bode Plot Phase Margin
35.	Pout	14.4 W	System	Total output power
36.	Vin	16.4 V	System	Vin operating point
37.	Vout	6.0 V	System	Operational Output Voltage

#	Name	Value	Category	Description
38.	Vout Actual	6.0 V	System Information	Vout Actual calculated based on selected voltage divider resistors
39.	Vout Tolerance	4.21 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
40.	Vout p-p	13.261 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	2.4	Maximum Output Current
SoftStart	2.0 ms	Soft Start Time (ms)
VinMax	16.4	Maximum input voltage
VinMin	14.8	Minimum input voltage
Vout	6.0	Output Voltage
base_pn	LMR14030S	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature
UserFsw	500.0 k	Customer Selected Frequency

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 14.8V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.


Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

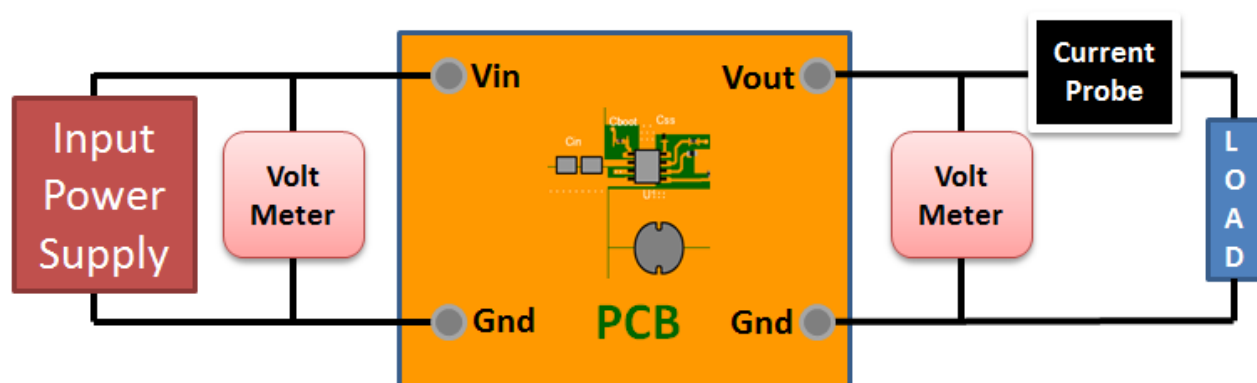


WEBENCH® Electrical Simulation Report

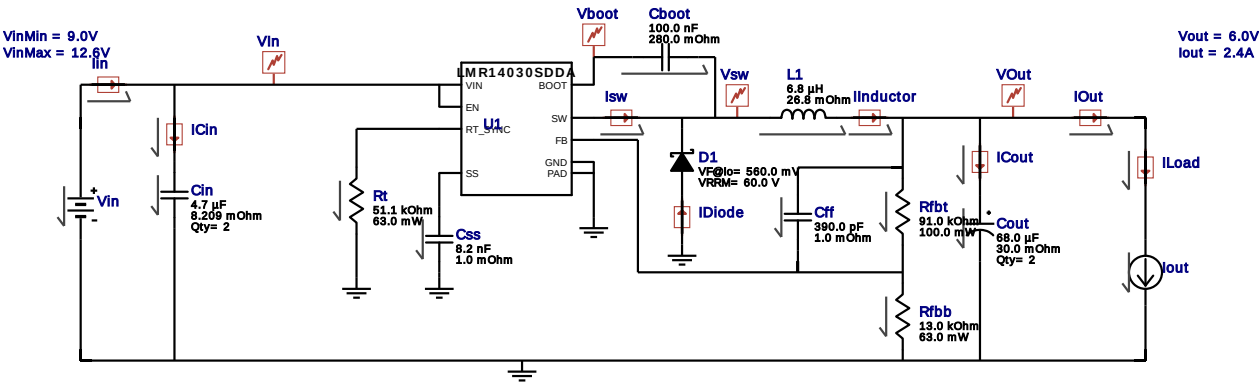Design Id = 1
sim_id = 1
Simulation Type = Steady State



Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	L1	IC	Initial Current	2.4 A
2.	Cboot	IC	Initial condition	10 V
3.	Iout	I	Load Current	2.4 A

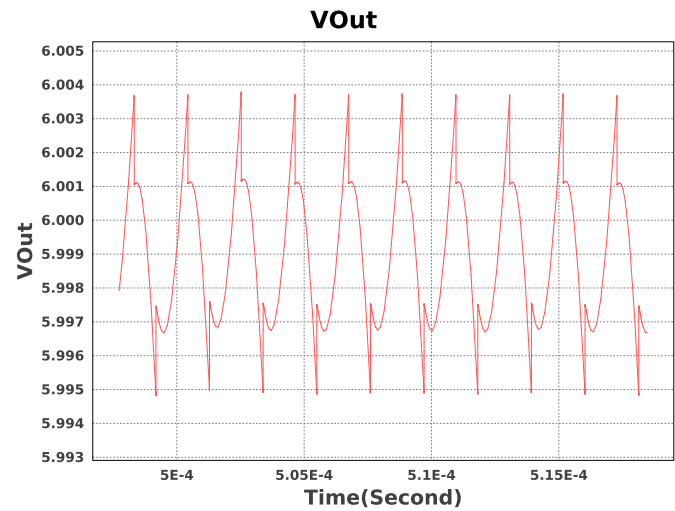

Design Assistance

- Master key : 39E66331F4444E9CA0EA904136A142C9[v1]
- LMR14030S Product Folder : <http://www.ti.com/product/LMR14030> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with TI products.